

Thevenin's Theorem Lab Procedure

Instructional Objectives

1. To work through the procedural steps involved in Thevenin's theorem.
2. To verify the values obtained by measuring them using the digital multimeter.
3. To construct a Thevenin equivalent circuit.

Procedure

0. Parts: 1-3.3K Ω , 1-6.2K Ω and 1-8.2K Ω .

We will run through 12 steps to use Thevenin's theorem to find the current through R3 shown in Fig. 5.

1. Building the circuit and doing measurements:

a. Measure R1, R2 and R3 using Digital Multi Meter (DMM)

R1 = ____3.262____K Ω , R2 = __8.115____K Ω , R3= ____6.110____K Ω

b. Setup the (YELLOW) power supply to deliver 5V DC with a 25mA current limit to the breadboard.

c. Build the circuit as shown in Figure 5.

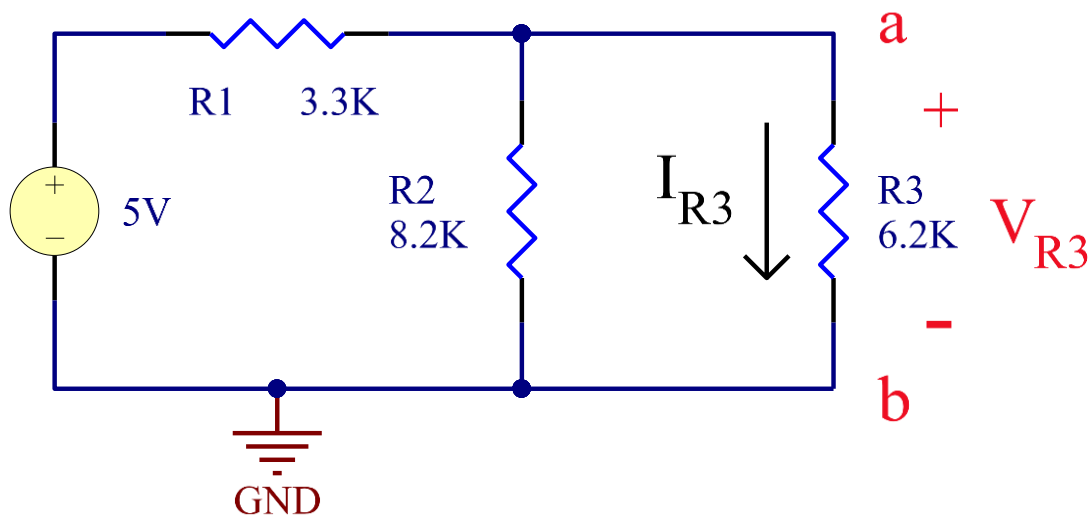


Figure 5

d. Measure the voltage across R3 (V_{R3}) using the DMM. Record the voltage and use the measured value of R3 to **Calculate** I_{R3} :

V_{R3} = _____2.585_____V

$I_{R3} = V_{R3} / R3 =$ _____0.423_____mA

Thevenin's Theorem Lab Procedure

2. Analyzing the circuit.

- a. Referring to Fig. 6, which is Fig. 5 with R3 removed, calculate V_{TH} for Fig.6, **showing/describing all work.**

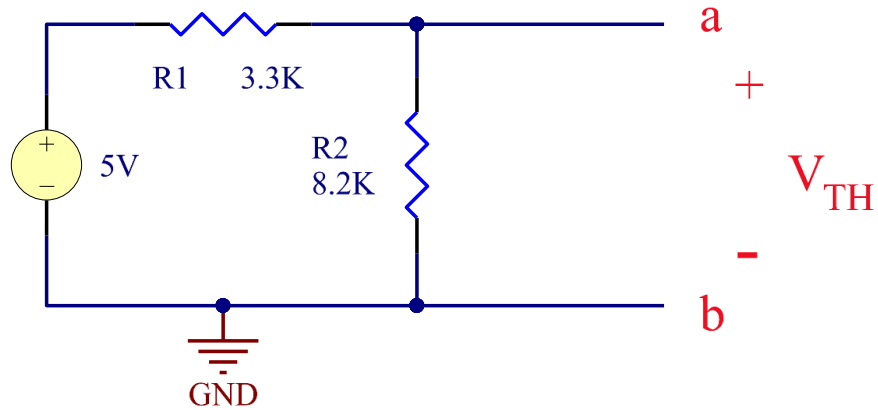


Figure 6

$$V_{th} = R_2 / (R_1 + R_2) * V_s = 8.2 \text{ K}\Omega / (3.3 \text{ K}\Omega + 8.2 \text{ K}\Omega) * 5V = 3.565V$$

b. $V_{TH} =$ _____ 3.565 _____ (calculated)

- c. Verify the real Thevenin equivalent voltage by measurement. Construct the circuit shown in Fig.6. Measure and record V_{TH} .

$V_{TH} =$ _____ 3.260 _____ (measured)

Thevenin's Theorem Lab Procedure

3. Measuring R_{TH} by removing the source and replacing it with a short circuit.

- a. Construct the circuit in Fig. 7, which is the circuit in Fig. 5 with R_3 removed and the 5V source replaced by a short circuit (R_{SOURCE} assumed 0).

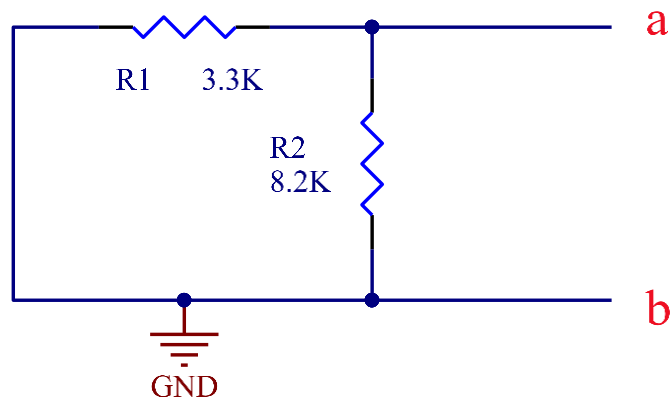


Figure 7

- b. Calculate R_{TH} in Fig. 7, **showing/demonstrating all work.**

$$R_{th} = R_1 \parallel R_2 = 1/(1/3.5 \text{ K}\Omega + 1/8.2 \text{ K}\Omega) = 2.353 \text{ K}\Omega$$

$$R_{TH} = \underline{\hspace{1cm}} 2.353 \underline{\hspace{1cm}} \text{ k}\Omega \underline{\hspace{1cm}} (\text{calculated})$$

- c. Verify your R_{TH} calculation by measurement. Connect the circuit in Fig. 7. Measure and record the equivalent resistance (R_{TH}) measured between terminals A and B.

$$R_{TH} = \underline{\hspace{1cm}} 2.125 \underline{\hspace{1cm}} \text{ k}\Omega \underline{\hspace{1cm}} (\text{measured})$$

Thevenin's Theorem Lab Procedure

4. Drawing the Thevenin equivalent circuit.

- a. Draw the Thevenin equivalent circuit and use your calculated values for V_{TH} and R_{TH} . **Label this Fig. 8.** You can use LTSpice or any other program to draw the circuit. Even a photo of a hand drawn picture.

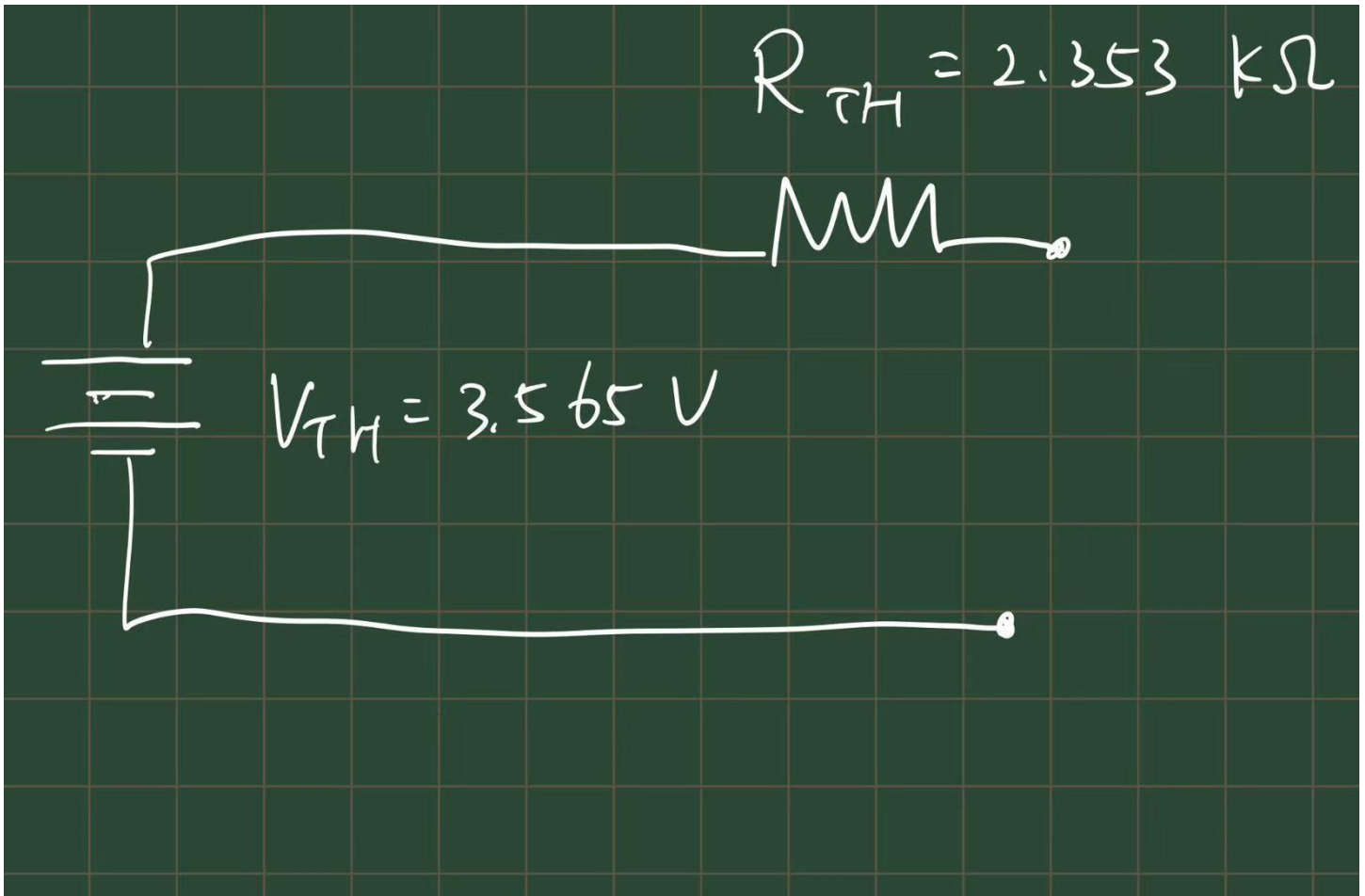


Figure 8

- b. With the Thevenin equivalent circuit loaded with R_3 , calculate I_{R3} using the Thevenin equivalent circuit from Fig. 8.

$$I_{R3} = \frac{V_{TH}}{R_{TH} + R_3} = 3.565V / (2.353 k\Omega + 6.2 k\Omega) = 0.417 \text{ mA} \quad (6)$$

- c. Compare the current calculated in procedure 1.d and the current calculated in procedure 4.b. Find the reasons for any discrepancy.

Thevenin's Theorem Lab Procedure

Result in 1d was 0.423 mA, and 4b gave 0.417mA. The discrepancy between calculated and measured is acceptable. The discrepancy can be due to factors like inaccuracies from manufacturing, creating non-ideal components, etc.

5. Building Thevenin equivalent circuit

a. Build the circuit of Fig. 8. Obtain a resistance for R_{TH} as close as possible to its calculated value. It doesn't have to be 1 resistor. Hint 2 resistors in parallel is 'real close'.

b. Measure the value of R_{TH} and V_{TH} using the DMM.

$R_{TH} = \underline{\hspace{1cm}} 2.125 \underline{\hspace{1cm}} \text{ k}\Omega$ $V_{TH} = \underline{\hspace{1cm}} 3.260 \underline{\hspace{1cm}} \text{ V}$

******* Load the Thevenin equivalent circuit with R3. *******

c. Measure the voltage across R_{TH} , (V_{RTH} not V_{TH}).

$V_{RTH} = \underline{\hspace{1cm}} 0.841 \underline{\hspace{1cm}} \text{ V}$

d. Measure the voltage across the load resistor R_3 (V_3)

$V_{R3} = \underline{\hspace{1cm}} 2.583 \underline{\hspace{1cm}} \text{ V}$

e. Calculate the current through R_{TH} and R_3 using measured values of V_{TH} , R_{TH} and R_3 (The resistors are in series so the same current flows through each of them).

$I = I_{R3} = V_{RTH} / R_{TH} = V_{TH} / (R_{TH} + R_3) \underline{\hspace{1cm}} 0.396 \underline{\hspace{1cm}} \text{ mA}$

f. Compare these measured results with the results of steps 4. Find the reasons for any discrepancies.

Calculated results from 4 gives $I=0.417 \text{ mA}$, while I from measured values is 0.396. The discrepancy is acceptable and is likely due to non-ideal measurement procedure.

g. Compare the current calculated in procedure 1.d and the current calculated in procedure 5.e. Find the reasons for any discrepancy

5e gave $I=0.396 \text{ mA}$, while theoretical value in 1d was 0.426 mA. Since the two circuits are theoretically equivalent, the discrepancy is likely due to non-ideal manufacture, or due to the measurement environment.

Thevenin's Theorem Lab Procedure

6. Complex Thevenin equivalent circuit

In this step, you are required to apply the Thevenin theorem to a more complicated circuit.

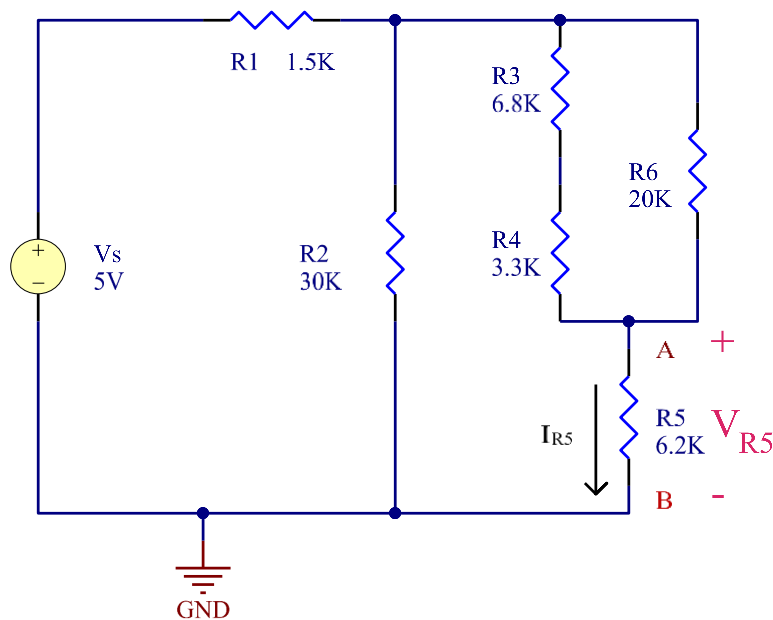


Figure 9

Using procedure explained in the theory section and/or your knowledge about finding a Thevenin equivalent, calculate the value of V_{TH} and R_{TH} for the circuit shown in Figure 9. Use R_5 as the load resistance (i.e. R_5 is removed for calculating the value of R_{TH} and V_{TH}). You can use the LTSpice simulator to check your Thevenin equivalents for this circuit if you want to. BTW LTSpice can not directly give you Thevenin equivalent values.

a. $V_{TH} = \underline{\quad 4.762 \quad} V$

b. $R_{TH} = \underline{\quad 8.140 \quad} K\Omega$

Thevenin's Theorem Lab Procedure

7. Calculate the value of I_{R5} using the Thevenin Equivalent Circuit

$$I_{R5} = V_{th} / (R_{th} + R_{s}) = 4.76V / (8.14 K\Omega + 6.2 K\Omega) = 0.332mA$$

a. $I_{R5} = \underline{\quad 0.332 \quad} mA$

8. Implement the Thevenin Equivalent Circuit on the proto board and measure the voltage across $R5$ as shown in Figure 10. Pick the closest 5% resistor for R_{TH} .

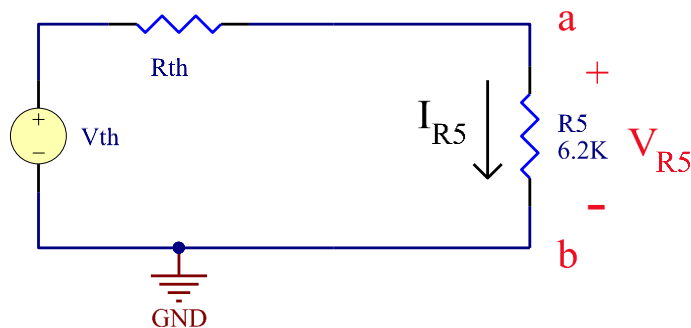


Figure 10. Thevenin equivalent of Circuit in Fig.8.

a. $V_{R5} \text{ (Measured)} = \underline{\quad 2.148 \quad} V$, $I_{R5} = V_{R5} / R_5 = \underline{\quad 0.352 \quad} mA$

- b. Does the value of I_{R5} match the calculated value in Part 7a?

Yes!

Post Lab Questions

1. What is meant by the word "equivalent" in Thevenin Equivalent circuits?

It means a theoretical equivalency in values of the **I-V relation** between the two terminals of a Thevenin circuit and that of the original.

Thevenin's Theorem Lab Procedure

2. What is the practical value of Thevenin Equivalent circuits? Give several practical applications in which Thevenin Equivalent circuits are used.

It reduces the complexity of linear circuits, and help focus on the load behaviour. It is particularly helpful in applications like power supply design.