

Operational Amplifiers Procedure

Instructional Objectives

1. Assemble a non-inverting amplifier circuit with an op-amp and measure the transfer function or gain of the output voltage with respect to the input voltage of the circuit.
2. Look at some parameters of a real op-amp.
 - a) Measure the output current limit of **real** op amp.
 - b) Observe clipping limitations of the op amp when used with AC or DC inputs.
3. Determine a 'reasonable' range for the resistances and gains used for op-amp circuits as dictated by the **real** op-amp.

Procedure

Components needed:


1 - 1K, 3 - 100K, 2 - 1K Ω , 2 - 3.3K Ω , 1 - 100K Ω , 1 - TLV271 OpAmp, 2 - 0.1uF ceramic capacitors.

0. Make sure you have looked at the Inverting and Non-Inverting amplifier configuration in the theory section.

STOP: Read the PowerSupplyDesc.docx now

It explains how to setup the power supply for this lab!

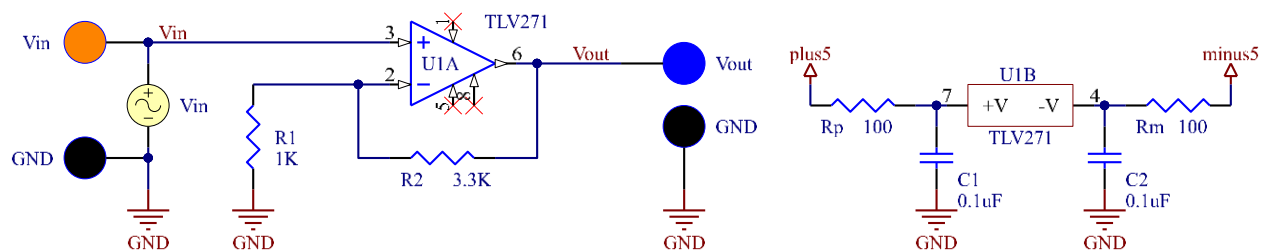1. Assemble the circuit shown in Fig. 1 on a breadboard. This is a non-inverting amplifier circuit as described in the theory section. Note the op-amp you will use in the lab has 8 pins. The schematic has the 8 pins shown with 2 distinct bodies. This is done to make the schematic easier to understand. The power supply is separated from the op-amp proper. In the schematic, pins 1, 5 and 8 have small X's on them. This means those pins are not connected to anything.



2.

Figure 1: Schematic of a non-inverting amplifier

Use the picture in figure 2 as a construction guide. It is just a guide don't consider it as the only way you can make it. The schematic in Figure 1 is the real circuit. Fig 2 however the recommended way to minimize errors. The errors will slow down the completion of the lab so minimize the possibility of them.

- Pin 1 of the op-amp is usually marked with an indented circle. The data sheet always indicates how to find pin 1 and which way the pins are numbered around the physical part.
- In Fig 2: The +5 and -5 volt power supplies are the red and blue mini clips connected to the 100 ohm resistors on the red and blue buses near the outer edge of the breadboard. They are the vertical buses that run the whole length of the board. I use Red for +5V and Blue for -5 volts. The bus next to it is usually GND. The +5 and -5 come from the + and - 30V supplies set to 5V. Note if Tracking is turned on you will see that the -30V supply will automatically be set to -5V when the +30V supply is set to +5V. **IMPORTANT: The 2 power supplies have to be connected correctly to create the circuit GND. See article on the Power Supply Desc.**

Operational Amplifiers Procedure

- I use two of the vertical buses on the breadboard as GND. The blue bus next to the +5V red bus line and the red bus next to the blue -5V bus. There is a black wire that connects the GND on one side to the GND on the other side.

NOTE: If you are confident you can correctly connect the power supplies directly to pins 4 and 7 of the op-amp you can omit the 100Ω resistors, R_P and R_M . They are only there to protect the op-amp if it gets connected incorrectly. The op-amp will most likely burn out if it is not connected to the power supplies correctly.

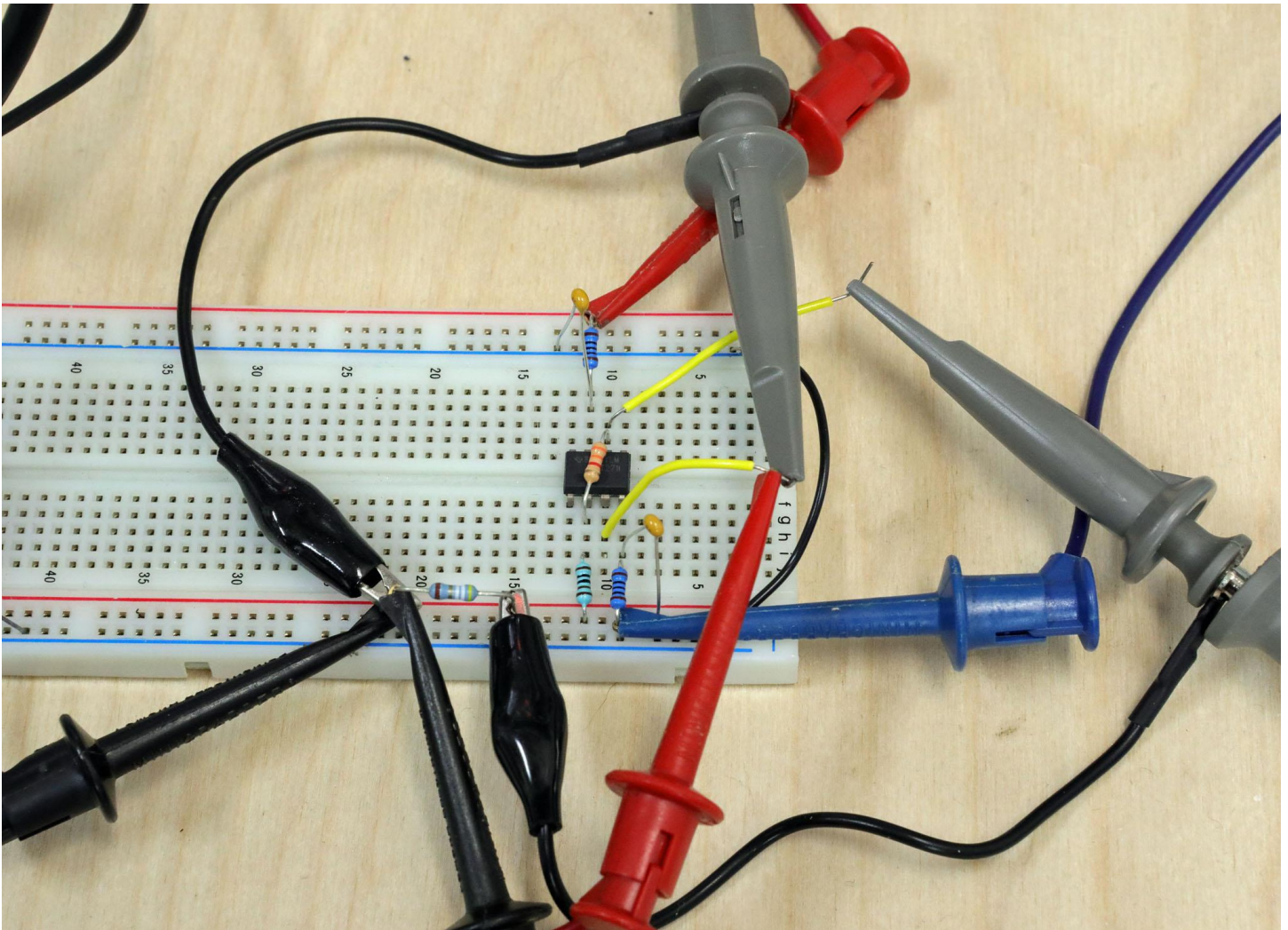


Figure 2: Non-Inverting Amp with Gain Prototype Example.

Note that there is a plus 5V DC source connected to pin 7 of the op-amp through a 100Ω resistor (Red clip) and a minus 5V source connected to pin 4 through a 100Ω resistor (Blue Clip). Any op-amp always needs external power. The TLV271 will not work without supplies. The 100Ω resistors are not usually needed. We are using them so if there are any mistakes in the building of the circuit the op-amp won't self-destruct. You don't really need them if you are confident the power supplies are properly connected.

Note: The two $0.1\mu\text{F}$ capacitors connected to pins 4 and 7 are usually referred to as bypass capacitors. The bypass capacitors are your friends. Always use them with op amp circuits! One of the benefits of using these is they prevent the op-amp circuit from oscillating (self-generating a high frequency at the output).

Operational Amplifiers Procedure

Equipment setup:

1. You will use 3 distinct pieces of equipment.
 - The Power Supplies are the +30V and -30V supplies set to +5V and -5V respectively. I strongly suggest you set the current limit on both channels of the power supply to 0.025A. This will save your op-amp from blowing up if it gets hooked up incorrectly.
 - Remember that using tracking on the power supply means you only have to set the +5V voltage.
 - The Signal Generator is the Wav Gen on the scope for V_{in} .
 - Red mini clip. No voltage yet. Use the BNC to mini clip cable for this.
 - The Oscilloscope will be used to measure up to 4 signals during lab.
 - CH1 to V_{in} and GND.
 - CH2 to V_{out} and GND.
 - CH3 and CH4 to other signals and GND.
 - Enable the outputs on the supply where the +5 and -5 V and common GND connected.
 - The power supply will indicate what voltage the + and - 30V supplies are at once turned on. Make sure they are somewhere near 5V in magnitude.
 - If the either voltage is low you probably have a short circuit that must be fixed. You may have ruined the op-amp. Figure out what is wrong and see if it works after correcting the mistake(s).

Always look at the V_{out} on the scope. It is a great way to make sure the circuit is still working after changes are made. This will also speed up lab completion. You will catch errors early and fix them in a timely manner.

What is the theoretical gain, $A = V_{out}/V_{in}$, of the circuit shown in Fig.1? $A = \text{Gain}$ 4.3 V/V

3. **Use the DMM** to measure V_{in} and V_{OUT} for the different DC V_{IN} voltages listed in Table 1 using the circuit shown in Fig. 1. Use the DMM on DC for these measurements. Remember you must set the Wav Gen to put out DC corresponding to the DC input voltages as you go.

V_{IN} Desired	Measured V_{in}	Measured V_{OUT}	$V_{in} \cdot A$ Theoretical	V_{IN} Desired	Measured V_{in}	Measured V_{OUT}	$V_{in} \cdot A$ Theoretical
0 V _{DC}	2.00 mV	6.93 mV	3.40	-0.5 V _{DC}	-0.501V	-2.135V	4.27
0.5 V _{DC}	0.50V	2.200V	4.241	-1.0 V _{DC}	-1.00V	-4.260V	4.256
1.0 V _{DC}	1.00	4.249V	4.247	-1.5 V _{DC}	-1.505V	-4.779V	3.056
1.5 V _{DC}	1.501V	4.802V	3.205				

Table 1: DC voltage measurements.

What is the gain A again? 4.3

Fill in the $V_{in} \cdot A$ Theoretical column in Table 1.

Did measured V_{out} always match $V_{in} \cdot A$? No What was V_{in} if it didn't? 0V, 1.5V, -1.5V

So what you just did was measure V_{out} and V_{in} for an op-amp circuit. 1 DC voltage at a time. This is not real efficient. There is an easier way to see the V_{out} and V_{in} signals with respect to each other.

- First you should use a waveform that moves linearly from the lowest voltage of interest to the highest.
- We are in luck there is a triangle waveform that does this.
- Set the signal generator to a 3V_{PP} 1KHz triangle wave with 0V offset and 50% Symmetry.
- The oscilloscope probes should be connected to V_{in} and V_{out} .
- Set the V_{in} sensitivity to 0.5V/Div and the V_{out} sensitivity to 2V/Div.
- Set the time base to 200uS/Div.
- You should see the input and output voltages appear on the screen. The output should be clipped.

Please note the scope settings are recommendations. You can change them if you want or need to.

Operational Amplifiers Procedure

MSO-X 2004A, MY53280120: Fri Nov 05 04:51:05 2021

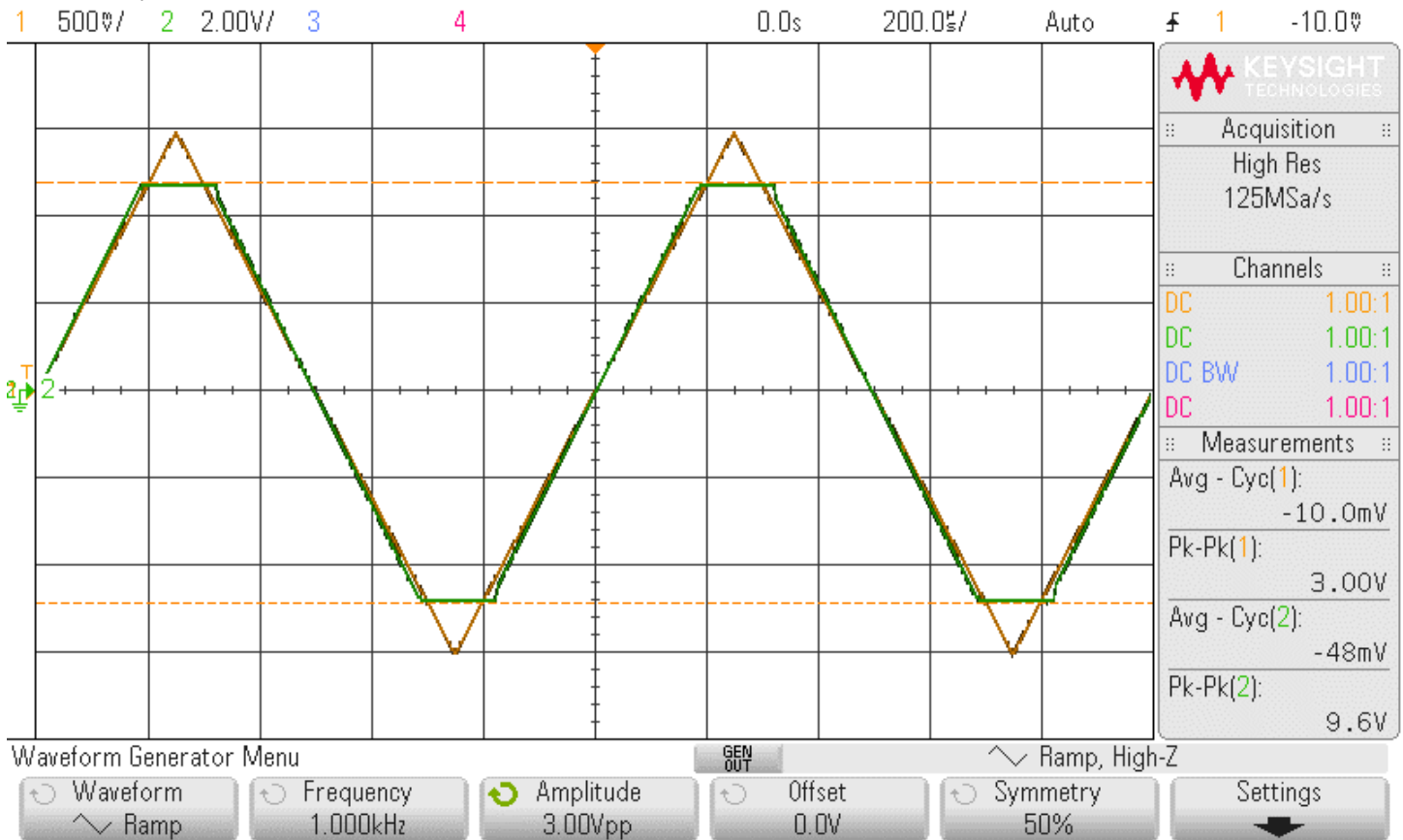


Figure 3: Triangle V_{in} (Yellow) and V_{out} (Green).

Next we will use the same circuit you built for the previous measurements. You will be adding a load resistor. You will be changing the load resistor during the next experiment. Just add the load resistor from pin 6 to GND on the breadboard.

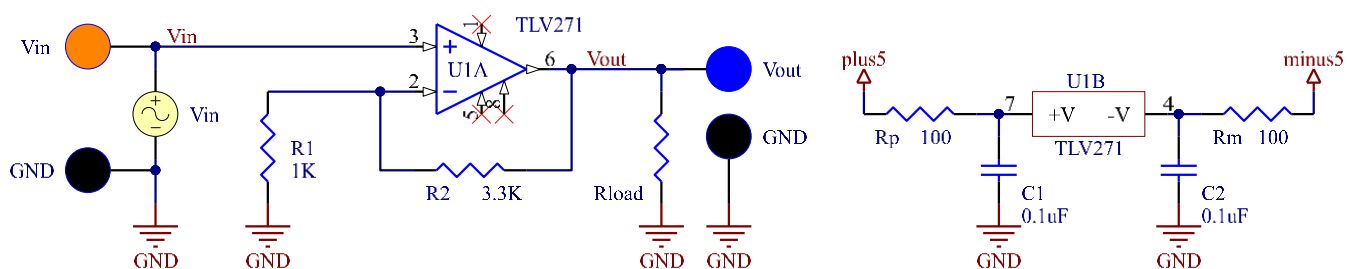


Figure 4: Non-inverting amplifier with gain and variable load resistor.

4. Qualitatively observe the output resistance of the op amp circuit shown in Fig. 4. This circuit is the same one in Figure 1 with the addition of a load resistor. In this case qualitative means: See if the output voltage changes when the load resistor changes. You will do this by measuring V_{OUT} with the scope.
 - Use the Oscilloscope to measure AC voltages and the DMM for DC.
 - Use a DC input first and secondly use a 1KHz **Sine** wave input for each R_{LOAD} .
 - Use R_{LOAD} as specified in table 2 for each test.
 - Use the 'Wavegen' trigger to hold the sine wave still.
 - Set V_{IN} to $1V_{DC}$ for the DC input or $2V_{PP}$ for a sine wave input of 1KHz. **NOTE:** Only input the AC or the DC not both at once.

Operational Amplifiers Procedure

- Measure the real value of R_{LOAD} with the DMM before you put it in the circuit and enter it in the Measured column of Table 2.
- Measure the voltages at V_{IN} and V_{OUT} as per Table 2 and enter the actual value next to the nominal value into the table. Use the Peak-peak measurement for AC and the DMM for DC measurements.
- Please note the output voltages will not change much until 100Ω .

Capture V_{OUT} with the AC input for $3.3K\Omega$ and 100Ω R_{LOAD} cases. A picture or USB key can be used for this.

R_{LOAD}		DC		1KHz sine wave	
Nominal	Measured	V_{INDC}	V_{OUTDC}	V_{INPP}	V_{OUTPP}
100K Ω	99.181Kohm	1V _{DC} 1.002V	4.370V	2V _{PP} 2.002V	8.27V
3.3K Ω	3.251 Kohm	1V _{DC} 1.002V	4.362V	2V _{PP} 2.002V	8.27V
1.0K Ω	997ohm	1V _{DC} 1.002V	4.245V	2V _{PP} 2.002V	8.30V
100 Ω	99.9ohm	1V _{DC} 1.002V	1.977V	2V _{PP} 2.002V	3.81V

Table 2. Measured data.

Op-amp output limit explorations: For now assume the op-amp is constrained by either a voltage limit or a current limit. Both limits look like the output voltage is limited when driving a resistor so first we will measure the voltage limit with no load resistor. No load so the op-amp is not delivering any current. In this state we will get the highest possible output voltage for the op-amp. Then we will ask for more current than the op-amp can deliver to measure the current limit.

5. Voltage clipping limits: Set V_{IN} to a 3V_{PP}, 1KHz sine wave with no offset. Using the circuit shown in Fig. 1, observe V_{OUT} on the Scope. Use $R_{LOAD} = \infty\Omega$ (No Load) . You will use the **scope** to measure the flattened (clipped) voltage levels.

MSO-X 2004A, MY53280120: Fri Nov 05 04:55:51 2021

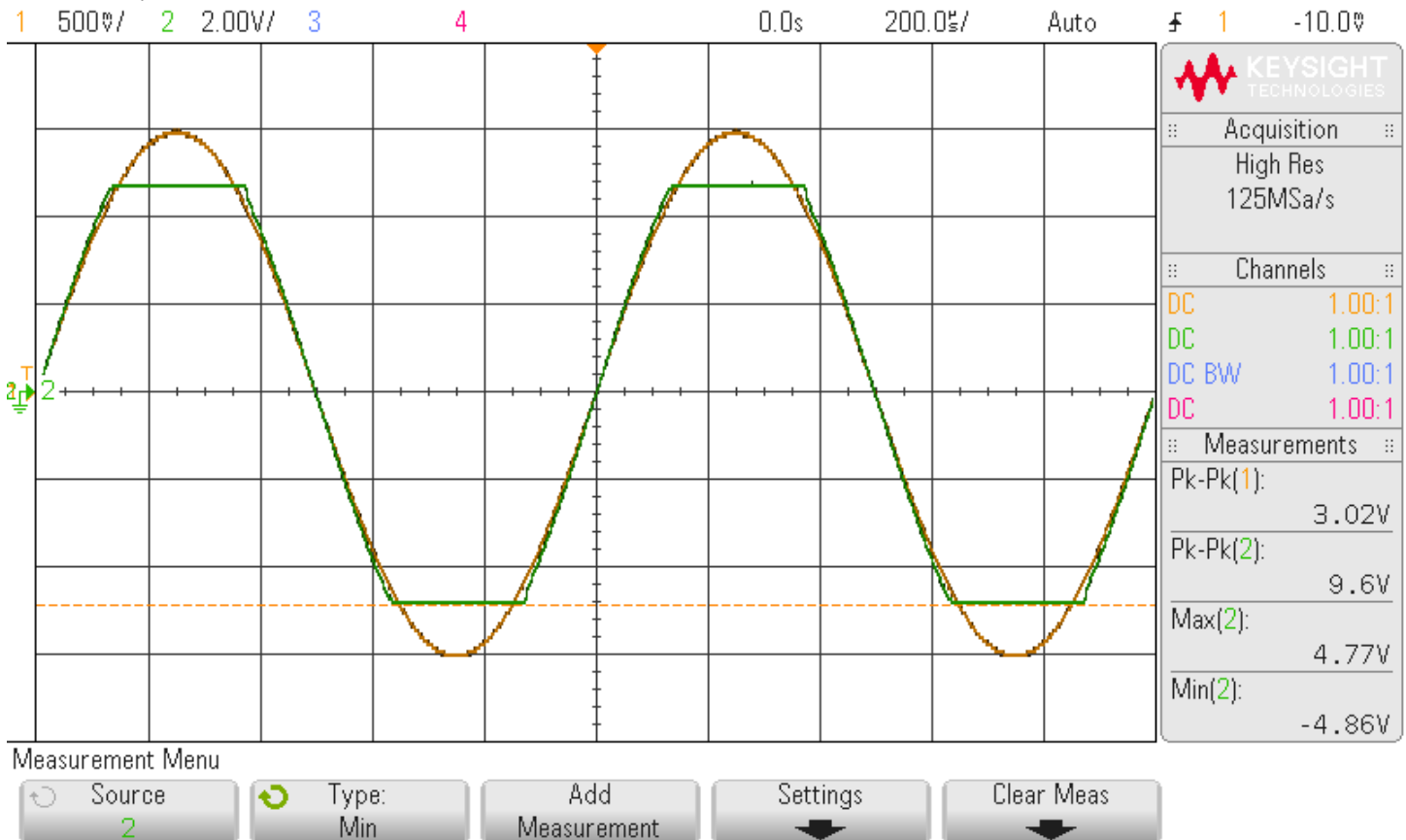


Figure 5: Clipped Vout display Vin Yellow and Vout Green..

Operational Amplifiers Procedure

6. I recommend that you use the Max and Min measurement to determine V_{HIGH} and V_{LOW} . Record the positive and negative voltage levels where V_{OUT} flattens out. The levels will be smaller in magnitude than the power supply voltages but close. This occurs because an op-amp can not put out a voltage outside of the power supply voltages.

$V_{OutClippedHighNoLoad}$ _____ 4.754V _____ $V_{OutClippedLowNoLoad}$ _____ -4.893V _____

7. Output current limit: Use the circuit from the Figure 4. Use an R_{LOAD} of 100 Ω .

First put a 2V_{PP} 1KHz sine wave in and look at the output with the scope. It should be clipping at a lower voltage than the voltage limits.

Next set V_{IN} to -1.0V_{DC}. Use the **DMM** to measure V_{OUTDC} . Copy the theoretical gain calculated above down here.

$A_{THEORETICAL}$ _____ 4.3 _____ V/V.

What should the output voltage be for the 1.0V_{DC} input? _4.36V_____.

At what positive and negative voltages should the circuit clip due to no load voltage limit measured above. ($V_{OutClippedXNoLoad}$)? pos _____ 4.27 _____ V, neg _____ -4.29 _____ V.

Measure the High voltage limit and Low voltage limit that you get when driving the 100 Ω resistor. Use $V_{in} = +1V_{DC}$ or $-1V_{DC}$.

$V_{IlimitOutHigh}$ _____ 1.943 _____ V, $V_{IlimitOutLow}$ _____ -1.948 _____ V.

Are the measured High and Low voltages smaller in magnitude than the no load clipping limits? _____ yes _____

So is the output voltage limited or current limited with the 100 Ω load? _____ current _____

Calculate the output currents by dividing the high and low voltage limits by R_{LOAD} (100 Ω).

$I_{IlimitOutHigh+}$ _____ 19.43 _____ mA, $I_{IlimitOutLow}$ _____ -19.48 _____ mA

8. **We are going to build a simple inverting amplifier with low gain.** The schematic is shown in Fig. 6. Determine the theoretical gain (Theory), V_{out}/V_{in} , of this circuit. $Gain_{LOW} =$ _____ -3.3 _____. Build this circuit on the breadboard. Since you got the circuit in Figs 1 and 4 running you- can skip using the 100 Ω current limiting resistors. They were there to prevent the destruction of the op-amp in case the circuit was built wrong. The assumption being you built it correctly and will this time too.

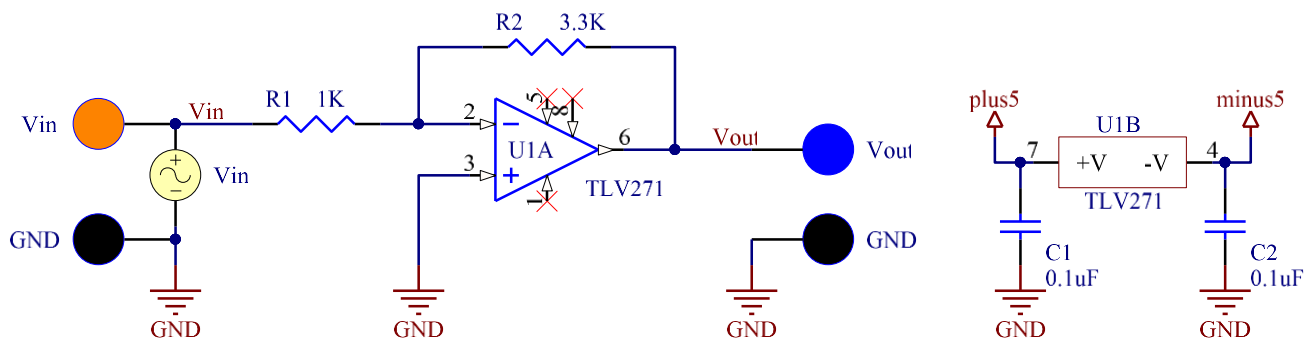


Figure 6: Inverting amplifier with low gain.

[illegible]

Figure 7: Inverting amplifier layout example.

- Set the input voltage V_{in} to $2.0V_{PP}$ at 200Hz with $0V_{DC}$ offset.
 - What should the theoretical DC output voltage be? _____ 0 _____ V_{DC} .
 - Note the AC input is $2.0V_{PP}$.
 - What should the AC output voltage be? _____ -6.6 _____ V_{PP} .
 - Monitor the AC output voltage with the scope. (Peak to peak Measurement) Measure the DC output with the DMM.
8. **Measure V_{in} and V_{OUT} .** to make sure the circuit is working as expected. Set the time base to about 1ms/div. Put the measured values in Table 3 for the Low gain row.

Review the theory section of the inverting amplifier. Make sure you understand what virtual ground means. Now connect the CH3 input to pin 3 of the op-amp. Pin 3 is connected directly to ground. The CH3 scope trace should be a straight line at 0V. Change the CH3 sensitivity to 1 mV/div. Is it still a straight line at 0V? For the next measurements. Put the CH4 probe on pin2 of the op-amp. Now measure the Pin2 (2) and pin3 (3) AC and DC voltages only with the scope. Only fill in the -3.3 Gain row right now. NOTE: If the output of the op-amp gets noisy try the X10 probe setting. Don't forget to change the probe setting on the scope too.

Operational Amplifiers Procedure

OpAmp Gain	200Hz 1V _P sine wave with 0V _{DC}							
	V _{inAC}	V _{inDC}	V _{OUTAC}	V _{OUTDC}	V _{3AC}	V _{3DC}	V _{2AC}	V _{2DC}
LOW (Fig 6)	980mV	0.025mV	-3.3V	0.870mV	-401mV	-0.004	-21mV	-0.126mV
HIGH (Fig 8)	Fill in later.							

Table 3:

Change R1 to 100Ω and R2 to 100KΩ as shown in Figure 8.

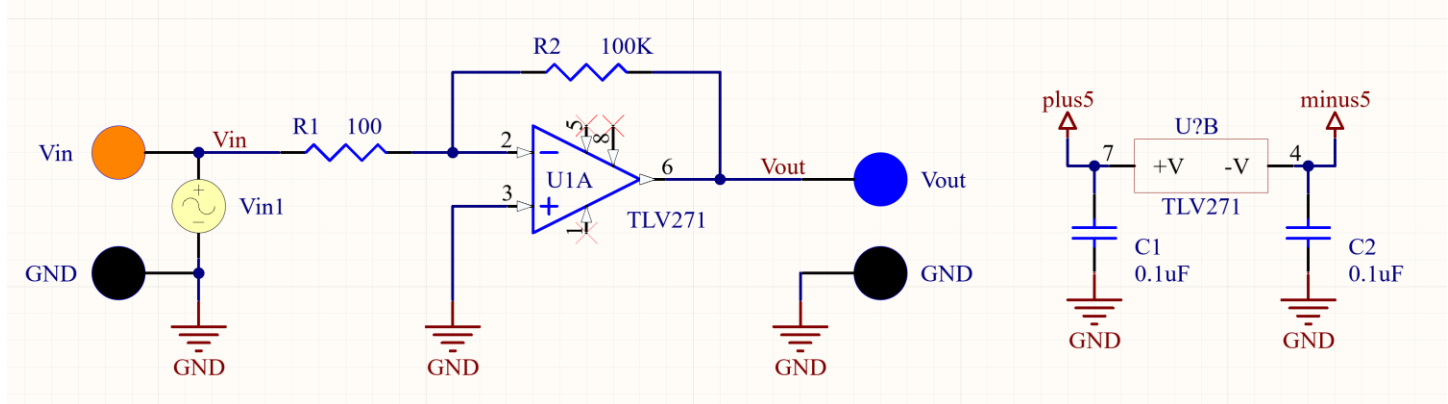


Figure 8: Inverting amplifier with high gain.

What is the theoretical gain, V_{out}/V_{in} , of this inverting amplifier? $\text{Gain}_{\text{HIGH}} = \underline{\quad -1000 \quad}$.

We want to put about in a 1 mV_{PP} V_{in} so that V_{out} will be 1 V_{PP}. We can't really do that with the existing signal generators so we need to do something special. We need to divide a 1V_{PP} signal down by about 1000 using a resistor divider. Fig 9. shows a scheme to do this division. This is usually called an attenuator.

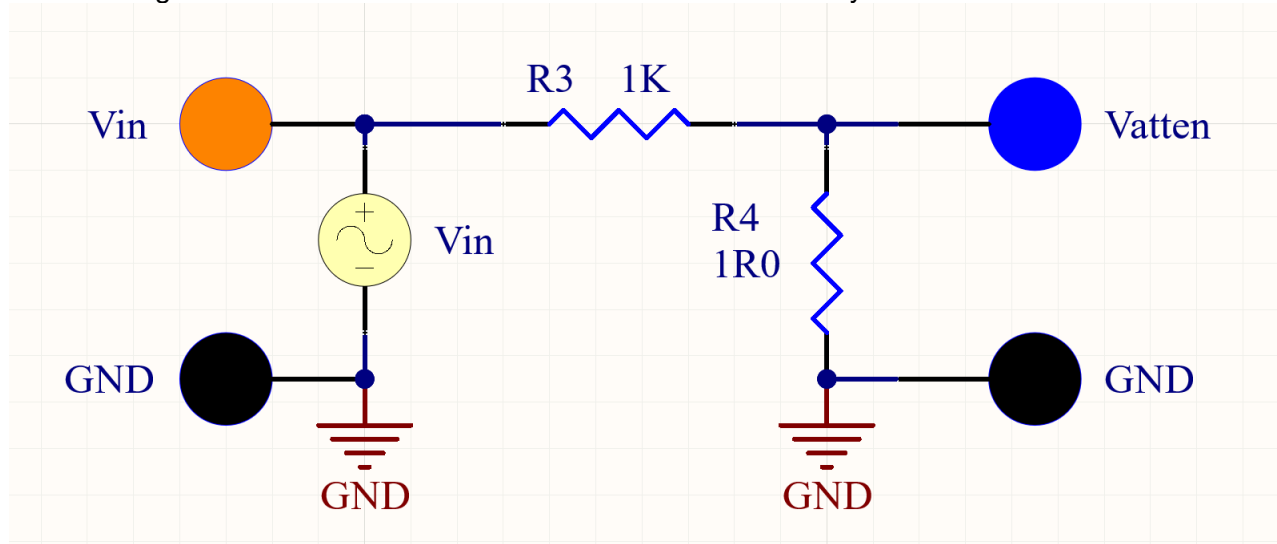


Figure 9: Resistor attenuator to generate a clean very low voltage.

Note the resistor marked 1R0 is a convenient way to list the value as 1Ω. The R takes the place of the decimal point (.). The R is much more visible than the decimal point so the value is clearly indicated this way.

What is the theoretical gain (It will be $\ll 1$) ? $\text{GAIN}_{\text{RESISTORS}} = \underline{\quad 9.999 \times 10^{-4} \quad}$

Note when gain is < 1 we sometimes use attenuation ratio which is the inverse of the gain.

Gain = V_{out}/V_{in} and Attenuation ratio is V_{in}/V_{out} . Again we usually call this little 2 resistor circuit an attenuator.

Operational Amplifiers Procedure

Connect in a $5V_{PP}$ 1KHz sine wave at V_{in} of the resistor divider. Connect CH1 from V_{in} to GND and connect CH2 from V_{out} to GND. Use the X1 setting on CH2 (V_{out}) if you aren't already. Adjust the CH2 sensitivity to 1mV / Div. Use the **Normal** "Acquire" mode.

Ch1 should be a nice clean sine wave. Ch2 looks like (pick 1) Good, **Bad** or Ugly google the phrase "The good the bad and the ugly".

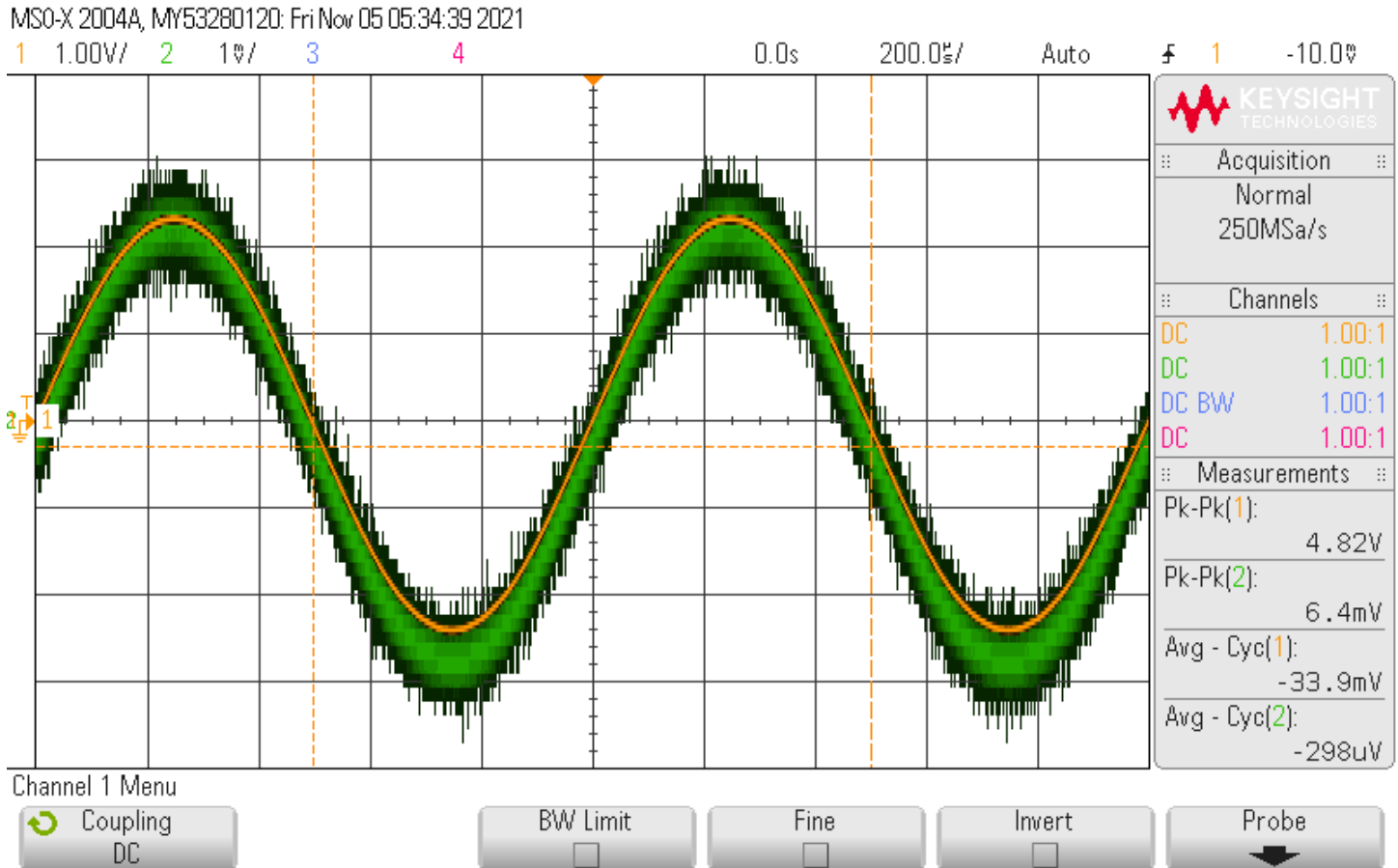


Figure 10: Attenuator signal voltages across each resistor. Yellow R3 and Blue R4.

Now use the **Average** mode of "Acquire" instead of Normal. I used 32 averages and got a pretty good trace. For Averaging to work you need to have a stable trigger so the sine wave is not moving. Use Wavegen triggering.

What is the approximate size of V_{in} and 4.83 V V_{OUT} 5.9 mV ?

Build the circuit shown in Fig.11. It is the attenuator in series with the high gain amplifier. What is the theoretical gain from V_1 to V_{out} ? $GAIN_{AMPLIFIER}$ 1000

Note the gain is for both AC and DC signals that are at V_{in} .

Operational Amplifiers Procedure

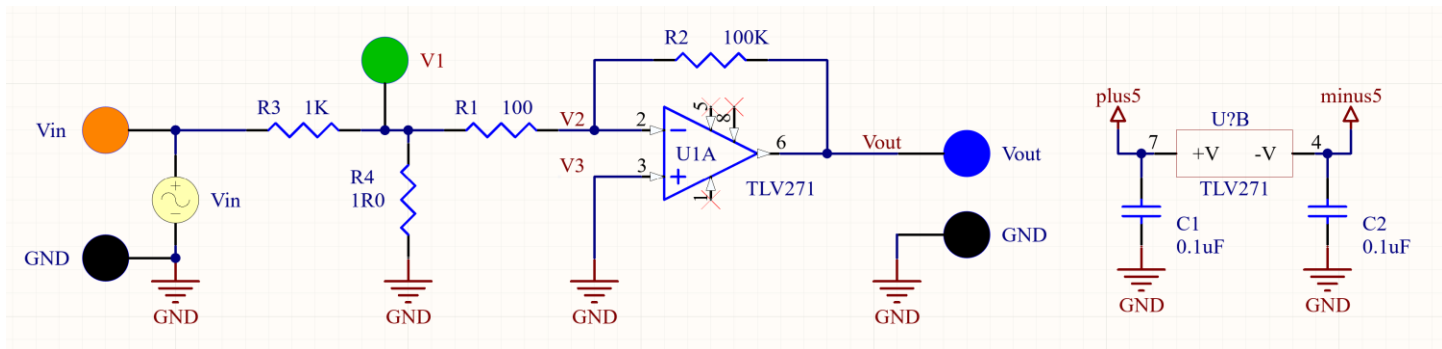


Figure 11: High gain inverting amplifier with attenuated input signal.

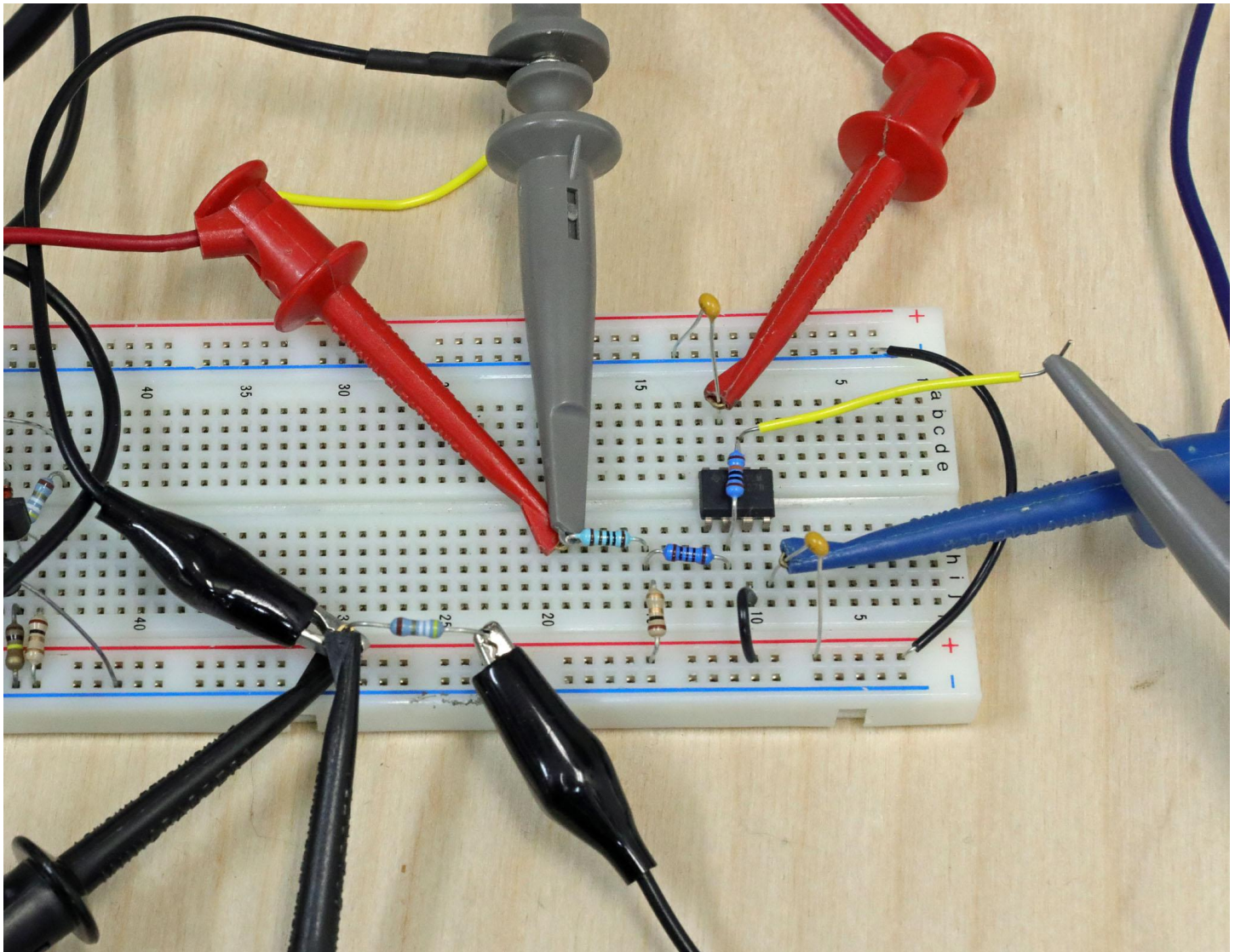


Figure 12: High gain inverting amplifier with attenuator layout example. This is similar to Fig 7 with R1 and R2 changed and R3 and R4 added.

What is the theoretical gain from V_{in} to V_{OUT} ? $GAIN_{ATTEN_W_GAIN} = \underline{\hspace{2cm}} 0.999 \underline{\hspace{2cm}}$

Hint: $GAIN_{ATTEN_W_GAIN} = GAIN_{RESISTORS} * GAIN_{AMPLIFIER} = V1/V_{in} * V_{out}/V1$

So anything at V_{in} should show up at V_{OUT} times $GAIN_{ATTEN_W_GAIN}$.

Operational Amplifiers Procedure

Set V_{in} to a 200Hz 5V_{PP} sine wave. Is the output a clean sine wave? yes

Remember Table 3 from above. Here it is again. Copy the values from above for the LOW gain row.

OpAmp Gain	200Hz 1V _P sine wave with 0V _{DC}							
	V_{inAC}	V_{inDC}	V_{OUTAC}	V_{OUTDC}	V_{3AC}	V_{3DC}	V_{2AC}	V_{2DC}
LOW	980mV	0.025mV	-3.3V	0.870mV	-401mV	-0.004	-21mV	-0.126mV
HIGH	1.01V	0.533mV	1.01V	1.403mV	1.63mV	0.051mV	20mV	1.431mV

Table 3: Again

Copy the info for the LOW gain entries from the previous table. Measure the data for the HIGH gain amplifier. Measure V_{in} and V_{out} first. Use the scope for AC and the DMM for DC. Then measure V_2 and V_3 with only the scope.

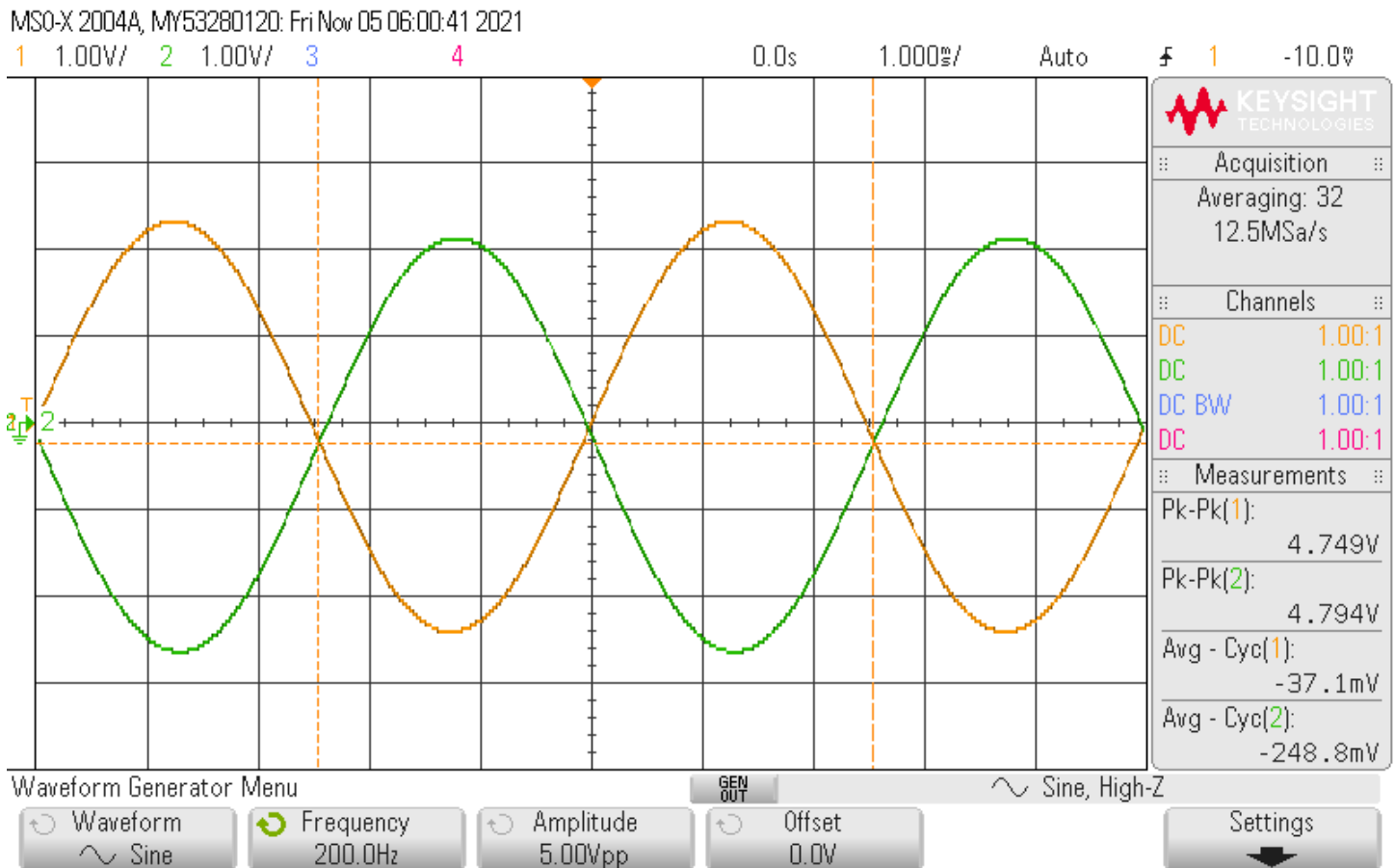


Figure 13: High Gain amplifier with attenuated input. V_{in} and V_{out} .

V_{inAC} and V_{OUTAC} should be about the same voltage. Remember: For V_2 and V_3 use the 1mV setting for CH3 and CH4 on the scope.

Is there anything suspicious about the waveform of V_{OUT} for the HIGH gain amplifier? Does it look different than it should in theory (Consider both the AC and DC output.)? YES

If yes what is "funny"?

Operational Amplifiers Procedure

There is probably a DC offset on the Vout signal. Where could that DC output voltage be coming from?

Is the DC offset of Vout the DC offset of $V_{inDC} * GAIN_{ATTEN_W_GAIN}$? Consider that. NO

- What is the DCOffset measurement of Vin (Use the DMM)? 0.508mV
- $V_{inDC} * GAIN_{ATTEN_W_GAIN} =$ 0.507mV.
- Measure the DC offset of Vout. V_{OUTDC} 1.421 V_{DC}
- Is that close to the V_{OUTDC} ? NO

Is it coming from the amplifier with a HIGH gain ? Consider that. YES

- Disconnect Vin from R3, the 1.0K resistor, and ground the R3 input. Use the DMM to measure Vout. What is V_{OUTDC} ? 1.421mV
- Is that close to the original V_{OUTDC} ? YES

Neither of these possibilities should be responsible for the DC offset at Vout. You have discovered one of the problems with using op-amp circuits with very high gain. In a real op-amp there is a small amount of dc offset between the In+ and In- terminals. With low gain circuits it doesn't really cause trouble. With high gain circuits it often causes trouble. To see what the DCOffset at the input terminals is you just take the V_{OUTDC} from table 3 and divide it by the gain. So if you got 1V DCOffset with a gain of -1000 the calculated input referred offset is $1V/(-1000)$ or -1 mV. We call this the input referred offset. What is the input referred offset for your -1000 gain amplifier? 1.4e-6 V


Unless you buy a special op-amp (expensive) that has very low input referred offset like say 10uV you will have a large DC offset in an op-amp when high gain is used.

Post Lab Questions

1. Plot the transfer function of V_{OUT} versus V_{IN} for the values you obtained in step 3, Table 1. Explain what is happening in the different regions of your plot.

We observe a linear relation between V_{in} and V_{out} as $V_{in} \sim 0$. But the relation distorts to nonlinearity as $V_{in} > 1$ or $V_{in} < -1$. As the input voltage increases, the output approaches the supply rails, where it can no longer increase linearly, causing the transfer function to flatten and deviate from a straight line.

Measured Vin	Measured VOUT
2.00 mv	6.93 mV
0.50V	2.200V
1.00	4.249V
1.501V	4.802V
-0.501V	-2.135V
-1.00V	-4.260V
-1.505V	-4.779V

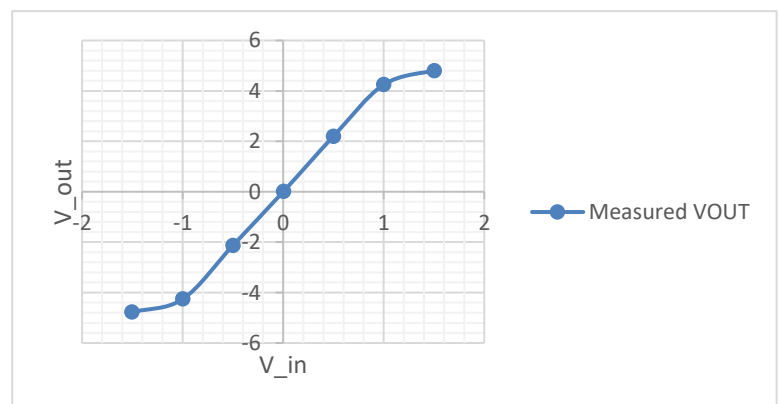

2. What are all the paths that the current coming out of or going into the output (pin 6) of the TLV271 for the circuit shown in Fig.4?

The current through R2 going into pin 6;
And the current out of the op amp.

Operational Amplifiers Procedure

3. What is the minimum load resistance (smallest resistive load) you can connect to the output so the current limit is reached just as the voltage clipping limit is reached? Choose the larger resistance of the positive or negative limits for the answer.

Min load resistance is around 220 Ohm