

Score: 60/60 Points 100 %

1.

Award: 13.33 out of 13.33 points

Calculate the value of $|H(\omega)|$ for the following values of H_{dB} .

(i) If $H_{dB} = 0.10$ dB, then $|H(\omega)| = \underline{1.0120}$ ✓.

(ii) If $H_{dB} = -3$ dB, then $|H(\omega)| = \underline{0.708}$ ✓.

(iii) If $H_{dB} = 210$ dB, then $|H(\omega)| = \underline{3.1620}$ ✓ $\times 10^{10}$.

References

**Numeric
Response**

Difficulty: Medium

Learning Objective: Understand the decibel scale, why we use it, and how to use it.

Calculate the value of $|H(\omega)|$ for the following values of H_{dB} .

(i) If $H_{dB} = 0.10$ dB, then $|H(\omega)| = \boxed{1.0116 \pm 1\%}$.

(ii) If $H_{dB} = -3$ dB, then $|H(\omega)| = \boxed{0.708 \pm 0.00101}$.

(iii) If $H_{dB} = 210$ dB, then $|H(\omega)| = \boxed{3.1623 \pm 1\%} \times 10^{10}$.

Explanation:

$|H(\omega)|$ is calculated as follows:

(i) 0.10 dB = $20\log_{10}|H(\omega)| \rightarrow |H(\omega)| = 1.0116$

(ii) -3 dB = $20\log_{10}|H(\omega)| \rightarrow |H(\omega)| = 0.7079$

(iii) 210 dB = $20\log_{10}|H(\omega)| \rightarrow |H(\omega)| = 3.1623 \times 10^{10}$

2.

Award: 13.33 out of 13.33 points

A series LR circuit is a lowpass filter if the output is taken across the resistor.

- ✓ ☒ True
☐ False

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R}$$

$H(0) = 1$ and $H(\infty) = 0$, showing that this circuit is a lowpass filter.

References

True / False

Difficulty: Medium

Learning Objective: Understand passive filters.

3.

Award: 13.34 out of 13.34 points

For a series LR circuit, calculate the corner frequency f_c if $L = 7$ mH and $R = 10$ k Ω .

The value of f_c for the series LR circuit is **227.36** ✓ kHz.

References

**Numeric
Response**

Difficulty: Medium

Learning Objective: Understand passive filters.

For a series LR circuit, calculate the corner frequency f_c if $L = 7$ mH and $R = 10$ k Ω .

The value of f_c for the series LR circuit is **227.36 ± 1%** kHz.

Explanation:

For a series LR circuit, we have

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R}$$

At the corner frequency, $|H(\omega_c)| = \frac{1}{\sqrt{2}}$, i.e.,

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega_c L}{R}\right)^2}} \quad \rightarrow \quad 1 = \frac{\omega_c L}{R} \quad \text{or} \quad \omega_c = \frac{R}{L}$$

$$\omega_c = \frac{R}{L} = 2\pi f_c$$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{10 \times 10^3 \Omega}{7.00 \times 10^{-3} H} = 227.36 \text{ kHz}$$

4.

Award: 10 out of 10.00 points

Design an active lowpass filter with a DC gain of -0.25 and a corner frequency of 500 Hz. Assume that $R_f = 20$ k Ω .

The value of R_i is 80  k Ω .

The value of C is 15.91  nF.

References

Numeric Response

Difficulty: Medium

Learning Objective: Understand active filters.

Design an active lowpass filter with a DC gain of -0.25 and a corner frequency of 500 Hz. Assume that $R_f = 20$ k Ω .

The value of R_i is 80 \pm 1% k Ω .

The value of C is 15.92 \pm 1% nF.

Explanation:

$$\text{DC gain} = -\frac{R_f}{R_i} = -\frac{1}{4} \quad R_i = 4R_f$$

$$\text{Corner frequency} = \omega_c = \frac{1}{R_f C_f} = 2\pi(500) \text{ rad/s}$$

If $R_f = 20$ k Ω , then $R_i = 80$ k Ω and


$$C = \frac{1}{(2\pi)(500 \text{ rad/s})(20 \times 10^3 \Omega)} = 15.92 \text{ nF}$$

5.

Award: 10 out of 10.00 points

Design the filter in the circuit given below to meet the following requirements:

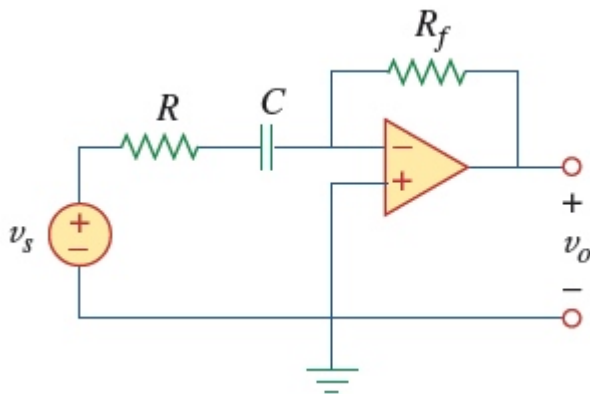- (a) It must attenuate a signal at 2 kHz by 3 dB compared with its value at 10 MHz.
- (b) It must provide a steady-state output of $v_o(t) = 10 \sin(2\pi \times 10^8 t + 180^\circ)$ V for an input $v_s(t) = 4 \sin(2\pi \times 10^8 t)$ V. Assume $R = 10 \text{ k}\Omega$.



The value of R_f in the circuit is 25 ✓ k Ω .

The value of C in the circuit is 7.96 ✓ nF.

References


**Numeric
Response**

Difficulty: Medium

Learning Objective: Understand active filters.

Design the filter in the circuit given below to meet the following requirements:

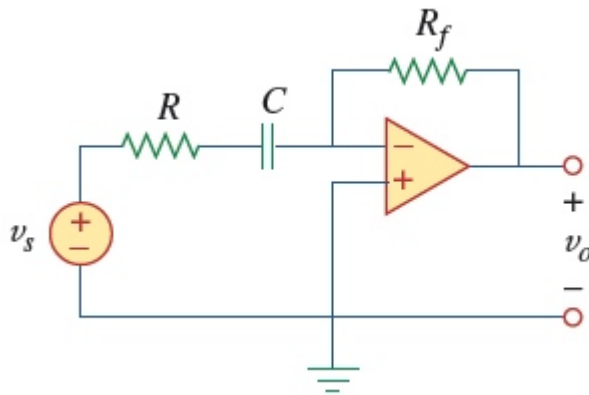- (a) It must attenuate a signal at 2 kHz by 3 dB compared with its value at 10 MHz.
- (b) It must provide a steady-state output of $v_o(t) = 10 \sin(2\pi \times 10^8 t + 180^\circ)$ V for an input $v_s(t) = 4 \sin(2\pi \times 10^8 t)$ V. Assume $R = 10 \text{ k}\Omega$.



The value of R_f in the circuit is $25 \pm 1\%$ k Ω .

The value of C in the circuit is $7.96 \pm 1\%$ nF.

Explanation:

This is a highpass filter with $f_c = 2$ kHz.

$$\omega_c = 2\pi f_c = \frac{1}{RC}$$

$$RC = \frac{1}{2\pi f_c} = \frac{1}{2 \times \pi \times 2 \times 10^3} = \frac{1}{4\pi \times 10^3}$$

10^8 Hz may be regarded as a high frequency. Hence, the high-frequency gain is

$$-\frac{R_f}{R} = -\frac{10}{4} \text{ or } R_f = 2.5R$$

If $R = 10$ k Ω , then $R_f = 25.00$ k Ω and

$$C = \frac{1}{(10 \text{ k}\Omega) \times (4\pi \times 10^3)} = 7.96 \text{ nF}$$